

Building Interactive Devices and Objects

Prof. Dr. Michael Rohs, Dipl.-Inform. Sven Kratz

michael.rohs@ifi.lmu.de

MHCI Lab, LMU München

Today


- I/O Ports and Buttons
- C for Microcontrollers
- Controlling Larger Currents
- Operational Amplifiers
- Sensors
- Analog-to-Digital Conversion
- USB-to-Serial Converter
- Exercise 3

Schedule

| # | Date | Topic | Group Activity |
|----|-----------|---|--------------------------------------|
| 1 | 19.4.2012 | Session 1: Introduction | Team building |
| 2 | 26.4.2012 | Session 2: Microcontrollers & Electronics | |
| 3 | 3.5.2012 | Session 3: Sensors | Concept development |
| 4 | 10.5.2012 | CHI | Concept development |
| 5 | 17.5.2012 | Christi Himmelfahrt | Concept development |
| 6 | 24.5.2012 | Session 4: Actuators | Concept presentation, Hardware requ. |
| 7 | 31.5.2012 | Session 5: Physical Objects (Sven) | |
| 8 | 7.6.2012 | Frohnleichnam | Project |
| 9 | 14.6.2012 | | Project |
| 10 | 21.6.2012 | | Project |
| 11 | 28.6.2012 | | Project |
| 12 | 5.7.2012 | | Project |
| 13 | 12.7.2012 | | Evaluation |
| 14 | 19.7.2012 | | Evaluation, Presentation |

Sessions 3: Sensors, Concept Development

 - Sensors, opamps, A/D-conversion
 - Potentiometer, IR distance sensors, capacitive, accelerometer
- Exercises
 1. Read potentiometer level to control LED blink rate
 2. Connect USB breakout board
 3. Concept development





Sharp GP2-1080 distance sensor

I/O PORTS AND BUTTONS

AVR I/O Ports

 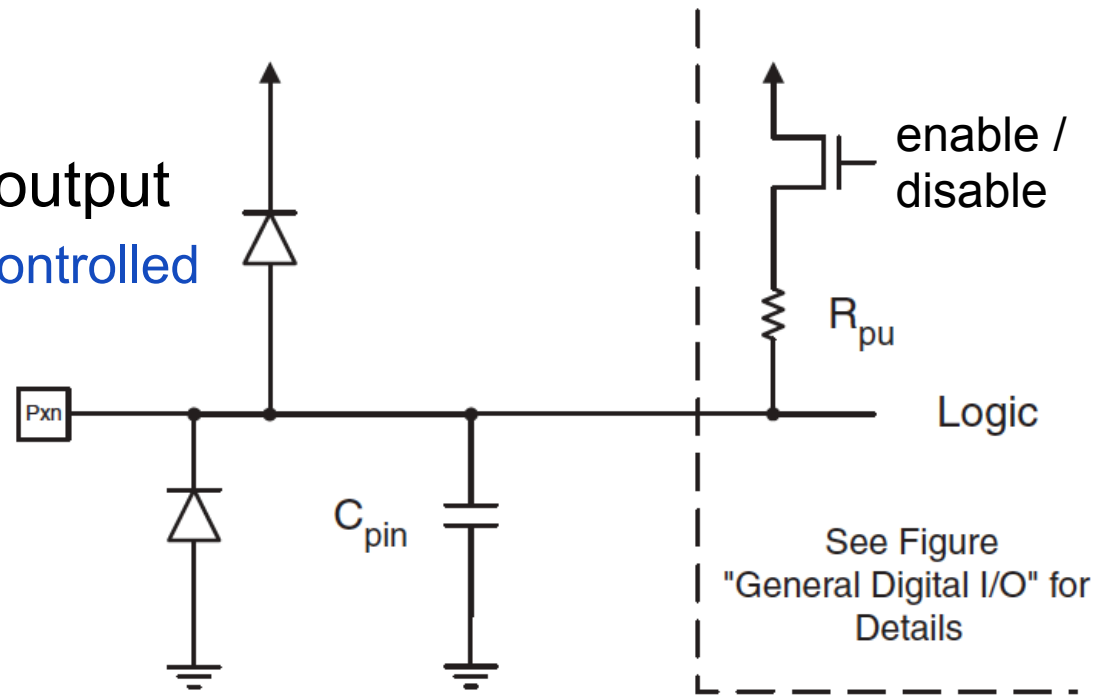
- I/O pin either input or output
 - Individually software-controlled
- Pin as output
 - States: low, high
 - Can drive 40mA (→ LED)
- Pin as input
 - Internal pull-up resistor (enabled/disabled in software)
 - high resistance state (high-Z) if pull-up disabled




Accessing the I/O Ports

- 3 memory addresses for each I/O port
 - Data Direction Register: $DDRx$
 - 1 = output
 - 0 = input
 - Data Register: $PORTx$
 - if output: 1 = PIN driven high, 0 = PIN driven low
 - if input: 1 = pull-up enabled, 0 = pull-up disabled
 - Port Input Pins: $PINx$
 - read: PIN state (independent of $DDRx$)
 - write 1: toggles $PORTx$

Output:

 

Input (pull-up enabled):

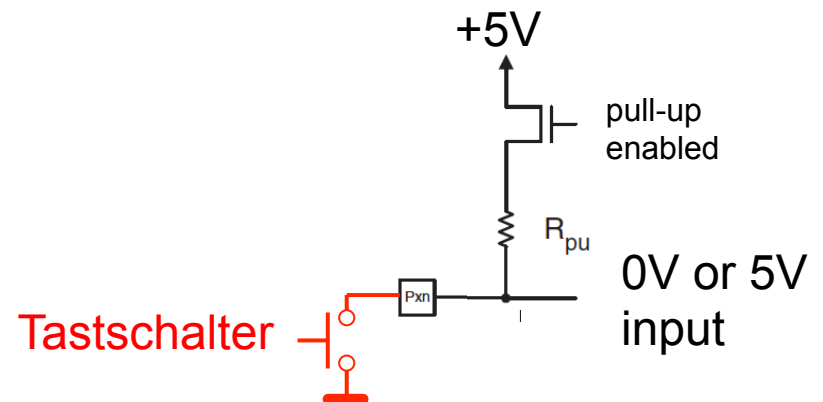

C FOR MICROCONTROLLERS

“The” C Book

- Kernighan/Ritchie:
The C Programming Language
- Imperative programming language
- Syntax resembles Java
 - `.java` → `.h` (declarations), `.c` (definitions)
 - no classes, no garbage collection, pointers
- C-Compiler compiles each `.c`-file separately into a `.o`-file
- C-Linker combines multiple `.o`-files and libraries into one executable file
- `make` (and `Makefile`) controls this process



The Preprocessor

- Before compilation, performs textual replacements
`#<preprocessor directive> [<argument(s)>]`
- Insertion of files (no duplicate checking)
`#include <avr/io.h>`
`#include "test.h"`
- Definition of constants
`#define MY_CONST 10`
- Conditions (often in header files to avoid duplicates)
`#ifndef MAIN_H_`
`#define MAIN_H_`
`unsigned char myFunction(unsigned char x);`
`#endif`

.h: Header files contain declarations

.c: Source files contain definitions

- test.h (declarations)

```
#ifndef TEST_H_  
#define TEST_H_  
unsigned char test(unsigned char i);  
#endif
```

- test.c (definitions, implementation)

```
#include "test.h"  
unsigned char test(unsigned char i) {  
    return 5 * i;  
}
```

C Data Types (for ATtiny, ATmega)

- signed char, 1 byte, -128..127
- unsigned char, 1 byte, 0..255
- signed int, **2 bytes**, -32768..32768
- unsigned int, **2 bytes**, 0..65535
- signed long, 4 bytes, $-2^{31}..2^{31}-1$
- unsigned long, 4 bytes, $0..2^{32}-1$

- ALU can only process 8-bits in parallel!
- avoid float and double!
 - emulated in software, large & slow

Bitwise Operations

- `&` and e.g. $0b11 \& 0b01 = 0b01$
 - `|` or e.g. $0b10 | 0b01 = 0b11$
 - `^` xor e.g., $3 \wedge 3 = 0$
 - `<<` shift left e.g., $5 \ll 3$ means $5 * 2^3$
 - `>>` shift right e.g., $5 \gg 1$ means $5 / 2^1 (=2)$
 - `~` not e.g., ~ 1 means $0xfe$
-
- very inexpensive operations

Declarations and Definitions of Variables

- Definitions reserves memory for the variable

```
unsigned char sharedVariable = 3;
```

(in main.c)

```
static unsigned char hiddenVariable = 2;
```

(in main.c, not accessible in other .c-files)

- Declarations describe the type but do not reserve memory

```
extern unsigned char sharedVariable;
```

(in test.c, refers to the variable in main.c)

- Similar use of **static** to limit accessibility of functions

```
static unsigned char test(unsigned char i);
```

(in main.c, not accessible in other .c-files)

Pointers

- Refer to a location in memory

```
int x[10];
```

```
int y;
```

```
int *p;
```

```
p = &x; // p points to first element (& = “address of”) x
```

```
y = *p; // y gets assigned x[0] (*p = “value at address p”)
```

```
*p = 0; // sets first element of x to 0
```

```
p = &x[1]; // p points to second element of x
```

- Pointer arithmetics

```
p = p + 1; // p points to next element
```

```
// (pointer value incremented by sizeof(int)=2)
```

- There are also pointers to functions!

Structs

- Example


```
struct point {  
    int x;  
    int y;  
}
```

- Usage

```
struct point pt;  
pt.x = 320;  
pt.y = 200;
```


- Structs are referenced by-value

 - example: `myFunc(struct point pt) ...`
puts 4 bytes (2 ints) on call stack




CONTROLLING LARGER CURRENTS

Multiplexing LEDs

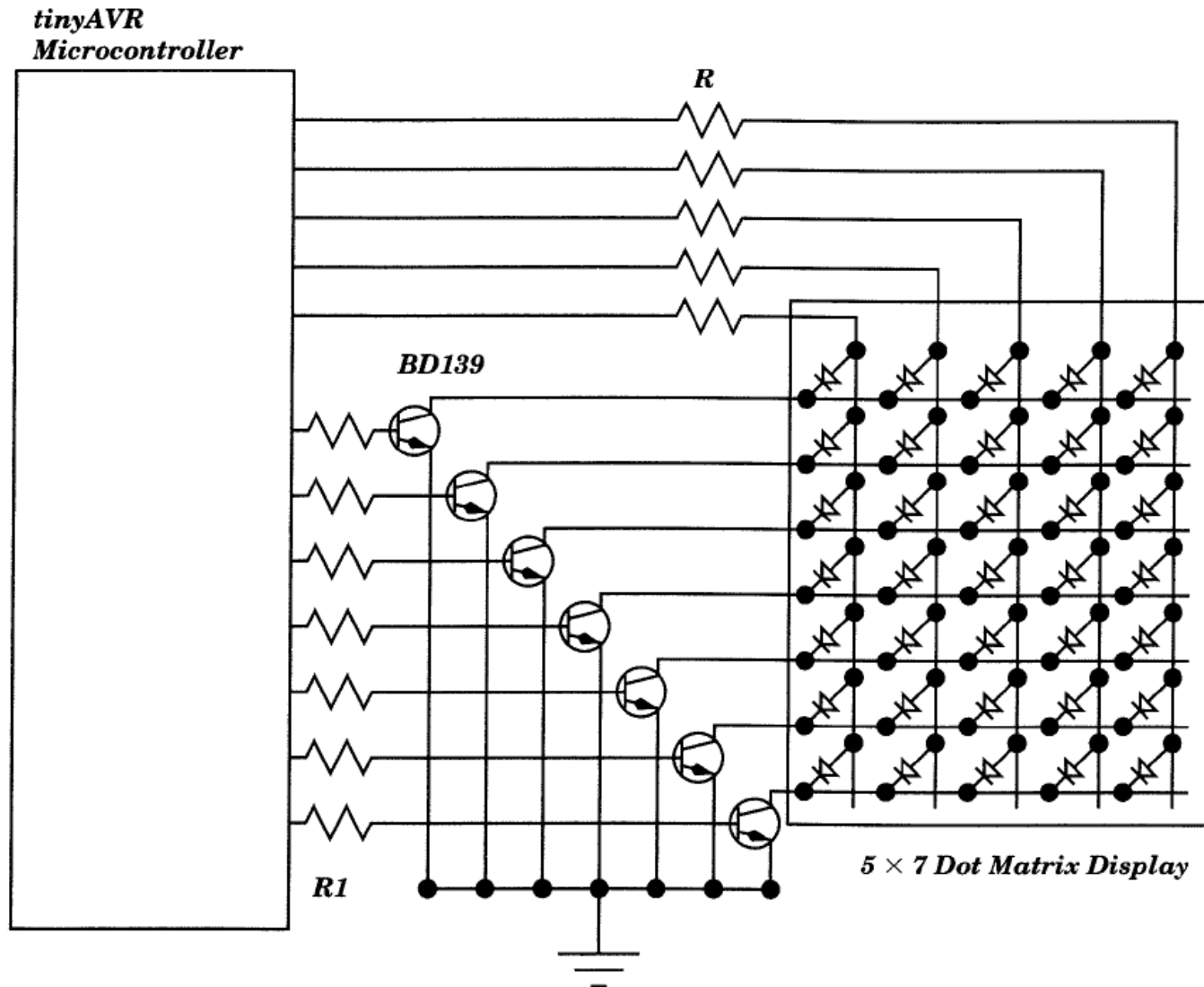

Source: Gadre, Malhotra: tinyAVR Microcontroller Projects for the Evil Genios. McGraw-Hill, 2011.


Driving More LEDs with a Transistor

 


- Given
 - $V_{CC} = 5V$
 - red LEDs: $U_F = 2V$, $I_F = 20mA$
 - BC548A: $I_{C,max} = 100mA$,
current gain $\beta = h_{FE} = 110..220$
- Drive 5 LEDs: 100mA
 - $h_{FE} = 120$ (@ $I_C = 100mA, V_{CE} = 5V$)
 - $V_{CE(sat)} = 0.2V$ (@ $I_C = 100mA, V_{CE} = 5V$)
 - $V_{BE(sat)} = 0.7V$ (@ $I_C = 100mA, V_{CE} = 5V$)
- R? R_B ?
 - $U_R = V_{CC} - V_{CE(sat)} - U_F$
 - $R = U_R / I_F$
 - $I_C = h_{FE} I_B$

Behavior of Transistors (active region)

NPN (e.g. BC548)

 

PNP (e.g. BC558)

 

- $I_C = h_{FE} I_B = \beta I_B$
- $I_E = I_C + I_B$
- $I_E \approx I_C$

Typical Characteristics of BC548

 


Figure 2. DC Current Gain vs. Collector Current

Source: Vishay Datasheet


 


Figure 7. Collector Saturation Voltage vs. Collector Current

Source: Vishay Datasheet

- $I_C = h_{FE} I_B = \beta I_B$
- $I_E = I_C + I_B$
- $I_E \approx I_C$

 EXAMPLE 1 Given $V_{CC} = +20\text{ V}$, $V_B = 5.6\text{ V}$, $R_1 = 4.7\text{ k}\Omega$, $R_2 = 3.3\text{ k}\Omega$, and $h_{FE} = 100$, find V_E , I_E , I_B , I_C , and V_C .



$$V_E = V_B - 0.6\text{ V}$$

$$V_E = 5.6\text{ V} - 0.6\text{ V} = 5.0\text{ V}$$

$$I_E = \frac{V_E - 0\text{ V}}{R_2} = \frac{5.0\text{ V}}{3300\ \Omega} = 1.5\text{ mA}$$

$$I_B = \frac{I_E}{(1 + h_{FE})} = \frac{1.5\text{ mA}}{(1 + 100)} = 0.015\text{ mA}$$

$$I_C = I_E - I_B \approx I_E = 1.5\text{ mA}$$


$$V_C = V_{CC} - I_C R_1$$

$$V_C = 20\text{ V} - (1.5\text{ mA})(4700\ \Omega)$$

$$V_C = 13\text{ V}$$

Source: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

 EXAMPLE 2 Given $V_{CC} = +10\text{ V}$, $V_B = 8.2\text{ V}$, $R_1 = 560\ \Omega$, $R_2 = 2.8\text{ k}\Omega$, and $h_{FE} = 100$, find V_E , I_E , I_B , I_C , and V_C .



$$V_E = V_B + 0.6\text{ V}$$

$$V_E = 8.2\text{ V} + 0.6\text{ V} = 8.8\text{ V}$$

$$I_E = \frac{V_{CC} - V_E}{R_1} = \frac{10\text{ V} - 8.8\text{ V}}{560\ \Omega} = 2.1\text{ mA}$$

$$I_B = \frac{I_E}{(1 + h_{FE})} = \frac{2.1\text{ mA}}{(1 + 100)} = 0.02\text{ mA}$$

$$I_C = I_E - I_B \approx I_E = 2.1\text{ mA}$$

$$V_C = 0\text{ V} + I_C R_2$$



$$V_C = 0\text{ V} + (2.1\text{ mA})(2800\ \Omega)$$


$$V_C = 5.9\text{ V}$$

Source: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

Transistors (larger current)

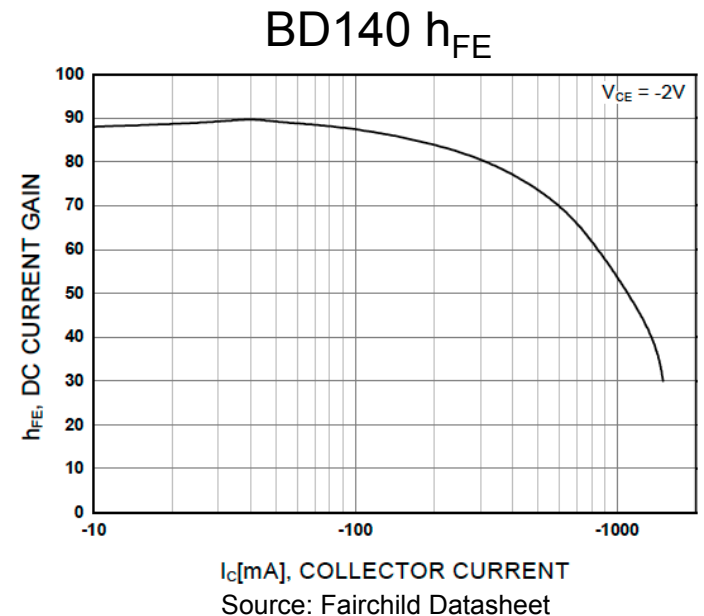 - BD139 – NPN
 - maximum ratings:
 $I_C = 1.5A$, $I_B = 0.5A$
 - $V_{CE(sat)} = 0.5V$, $V_{BE} = 1V$
 - $h_{FE} = 63..160$ @ $I_C = 150mA$, $V_{CE} = 2V$
- BD140 – PNP
 - maximum ratings:
 $I_C = -1.5A$, $I_B = -0.5A$
 - $V_{CE(sat)} = -0.5V$, $V_{BE} = -1V$
 - $h_{FE} = 40..250$ @ $I_C = -150mA$, $V_{CE} = -2V$




 

OPERATION AMPLIFIERS

Operational Amplifiers

 - Amplify signals (e.g. from sensors)
 - Differential amplifier
- Ideal op-amps
 - **Rule 1:** open-loop voltage gain: $A_O = \infty$
 - **Rule 2:** Infinite input impedance: $R_{in} = \infty$
 - **Rule 3:** Input terminals draw no current
 - *If negative feedback:* **Rule 4:** $V_+ - V_- = 0$



real op-amp

Ideal op-amp:


 


Figure author: Inductiveload, public domain


Real op-amp:

 


Op-Amps as Comparators

- Op-amp in open-loop setup (no negative feedback)
 - Ideal op-amp has open-loop voltage gain: $A_O = \infty$
 - Real op-amp voltage limited by supply voltage (V_{S-} , V_{S+})
 
$$V_{out} = \begin{cases} V_{S+} & V_1 > V_2 \\ V_{S-} & V_1 < V_2 \end{cases}$$



 - Used for setting voltage thresholds
 - Example: V_2 set to fixed reference voltage (voltage divider, potentiometer), V_1 attached to sensor, V_{out} either 0 or V_{CC}
- Dedicated comparator chips
 - Example: LM339



LM339, Source: TI Datasheet

Operational Amplifiers

- Op-amp circuit diagram


 - V_+ : non-inverting input

 - V_- : inverting input

 - V_{out} : output

 - V_{S+} : positive power supply

 - V_{S-} : negative power supply

 


© Omegatron, CC-BA-SA

- Negative feedback

 - Rule 4: $V_+ - V_- = 0$

 - Closed-loop operation

 - Used to control gain (V_{out}/V_{in})

 

© Ong saluri, CC-BA-SA

Unity Gain Buffer

- Gain: $V_{\text{out}} / V_{\text{in}} = 1$
- Benefits
 - high input impedance
 - low output impedance
- High input impedance
 - does not draw much current from source
- Low output impedance
 - drives load like a good voltage source

 


Figure author: Inductiveload, public domain

Inverting Amplifier

- $V_+ = V_- = 0V$ (rule 4)
- $I = V_{in} / R_{in}$ (Ohm's law)
- $-I = V_{out} / R_f$ (Ohm's law, rule 3)
- **Gain:**
 $V_{out} / V_{in} = - R_f / R_{in}$

 


Figure author: Inductiveload, public domain

 


Figure: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

Non-Inverting Amplifier

- $V_{in} = V_+ = V_-$ (rule 4)
 $= R_1 / (R_1 + R_2) * V_{out}$
(Ohm's law, rule 3)
- Gain:
 $V_{out} / V_{in} = (R_1 + R_2) / R_1$
 $= 1 + R_2 / R_1$

 


Figure author: Inductiveload, public domain


 


Figure: Paul Scherz: Practical Electronics for Inventors. 2nd edition, McGraw-Hill, 2007.

AVR ATtiny45 Architecture



- Analog Comparator

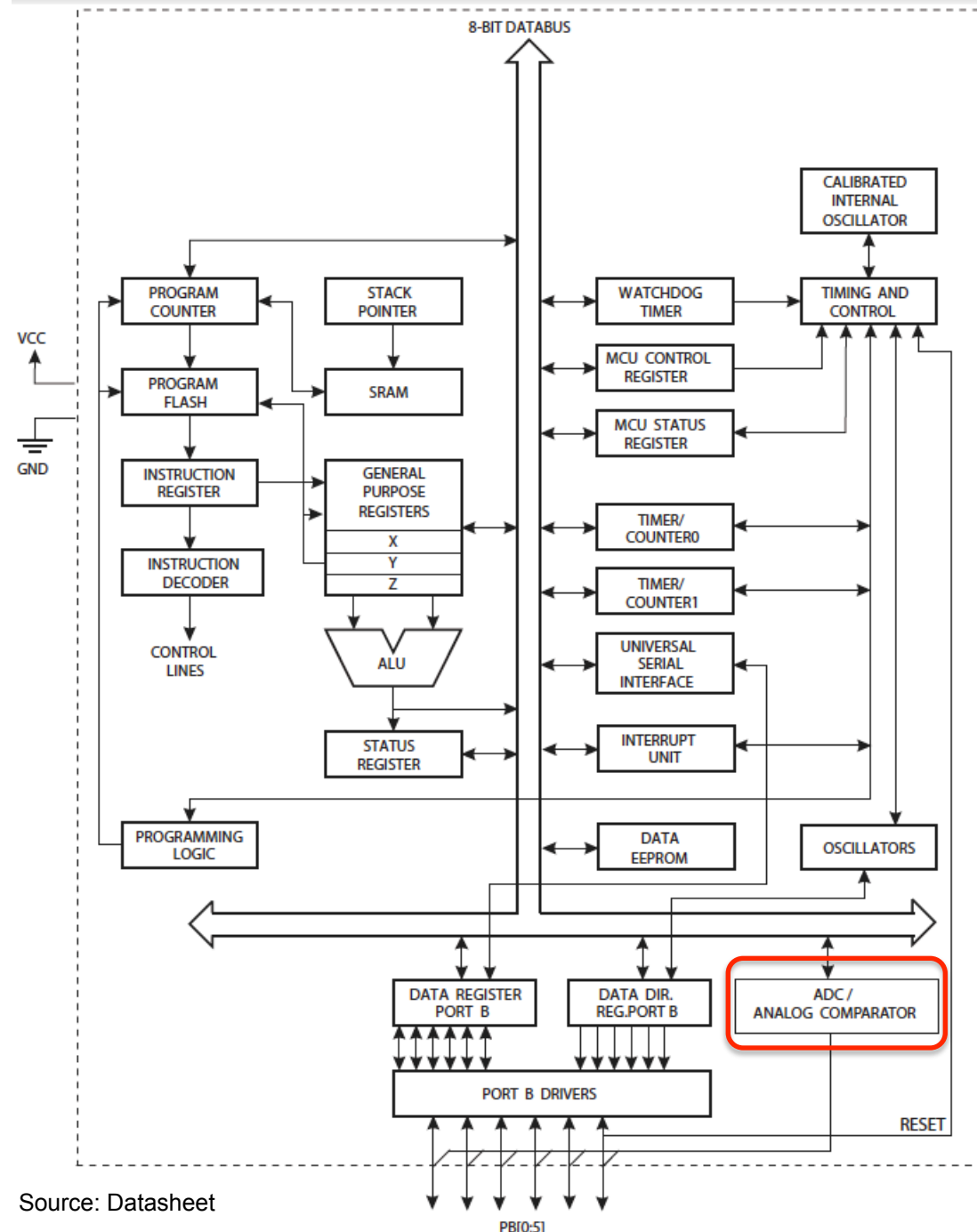

Source: Datasheet

ATtiny45 Analog Comparator

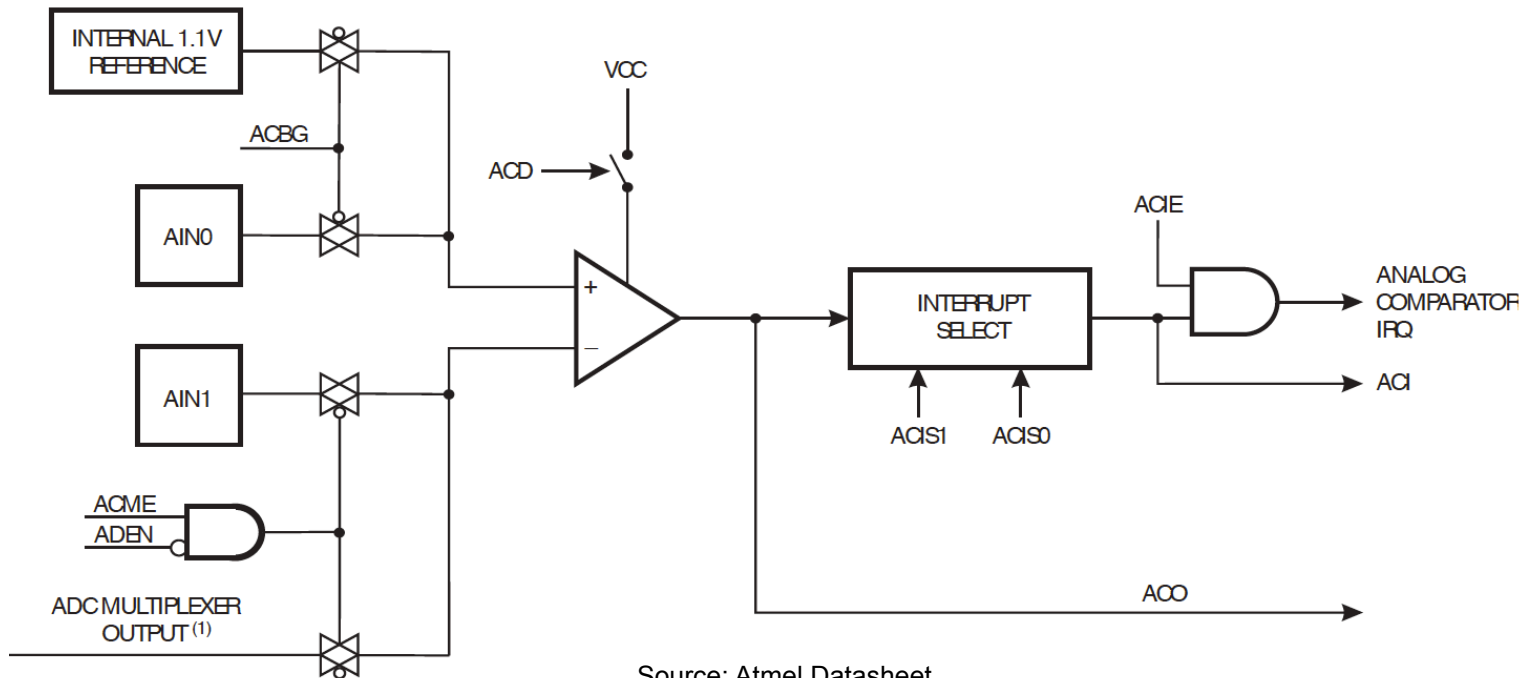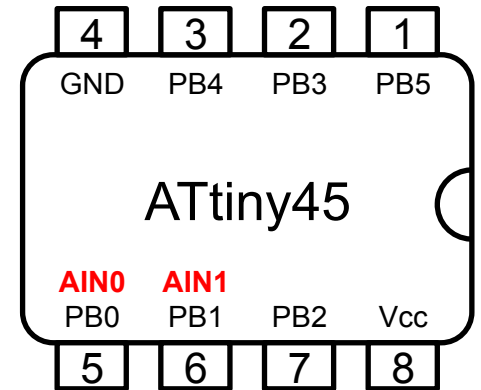- Compares inputs AIN0 (+) and AIN1(-)
- Sets ACO if AIN0 > AIN1
 - Can trigger interrupt (on ACO rise, fall, or toggle)
- Registers control comparator: ADCSRB, ACSR, DIDR0



Source: Atmel Datasheet



SENSORS

Encoding of Sensor Values

- Binary: GND-level or V_{CC}
 - simple
- Continuous voltage: $0..V_{CC}$
 - requires A/D conversion
- Frequency
 - requires counters
- I2C bus
 - requires implementation of bus protocol
- etc.



Buttons and Switches

  - Push buttons
 - Closed while pressed
- Toggle buttons
 - Change state when pressed
- Switches
 - Off position, on position
- Tilt Switches
 - Contains conducting ball contact
 - Contact closes based on gravity




Hall Sensor (TLE 4905)

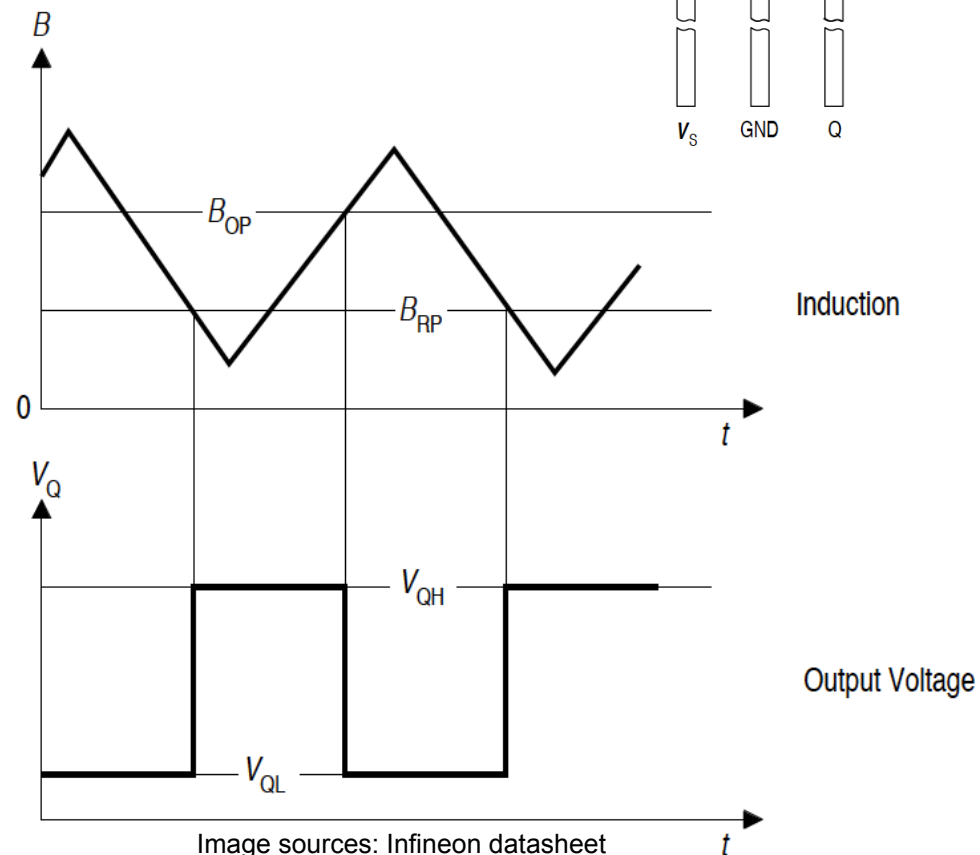 - Senses magnetic field: switch on, when magnet nearby
- Used in bike computers to count wheel revolutions
- Principle: Magnetic field perpendicular to Hall sensor induces voltage
- $V_S = 3.8..24V$
- $I_{out} = 100mA$




LEDs as Light Sensors

- LEDs are photo diodes
 - Sensitive to light at the wavelength they emit
 - Indirectly measure photo current
 - Use LED under reverse bias conditions
 - Anode to ground
 - Cathode to +VCC
-
- Dietz, Yerazunis, Leigh: [Very Low-Cost Sensing and Communication Using Bidirectional LEDs](#). UbiComp 2003, pp. 175-191.
 - Hudson: [Using Light Emitting Diode Arrays as Touch-Sensitive Input and Output Devices](#). UIST 2004, pp. 287-290.

 


Normal operation


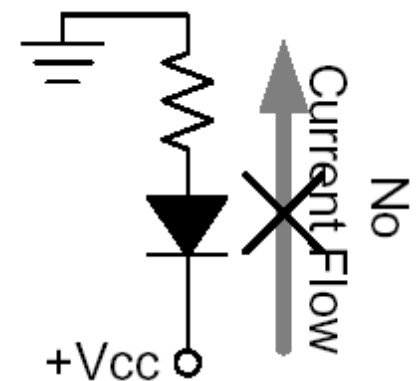


Reverse-biased LED


LEDs as Light Sensors

 

Reverse biased LED

  

 Modeled as capacitor in parallel with current source (photocurrent)




Circuit for light sensing

- Reverse biased LED = Capacitor parallel to photocurrent
- Sensing algorithm
 - Set microcontroller pin to high → capacitor charges
 - Switch pin to input mode → photo current discharges capacitor
 - Measure time until pin is low


LEDs as Light Sensors

```
unsigned int senseLight() {  
    // reverse bias LED  
    DDRB |= 0b00000001; // PB0 output  
    PORTB |= 0b00000001; // PB0 high  
    _delay_ms(10);  
  
    // put in high-Z state  
    DDRB &= 0b11111110; // PB0 0 input  
    PORTB &= 0b11111110; // PB0 low (turn off pull-up resistor)  
  
    // count until pin drops to low  
    unsigned int time = 0;  
    while ((PINB & 1) == 1 && time < 0xffff) {  
        time++;  
    }  
    return time;  
}
```

 

 
Exercise: Alternate between Emitting and Sensing Light

```
unsigned int senseAndEmitLight() {  
  
    // ...  
  
    return time;  
}
```




Capacitive Sensing

 - Sense change in capacity of a capacitor
 - Modified by presence of hand/finger
 - Also depends on air humidity
- Senses hovering hand/finger
 - Zero force
 - Through (thin) insulating materials
- Components
 - Aluminum or copper foil
 - Large resistor (100k Ω ..10M Ω)
- Algorithm
 - Change state of output pin
 - Measure delay in time of input pin (loop)



Capacitive Sensing

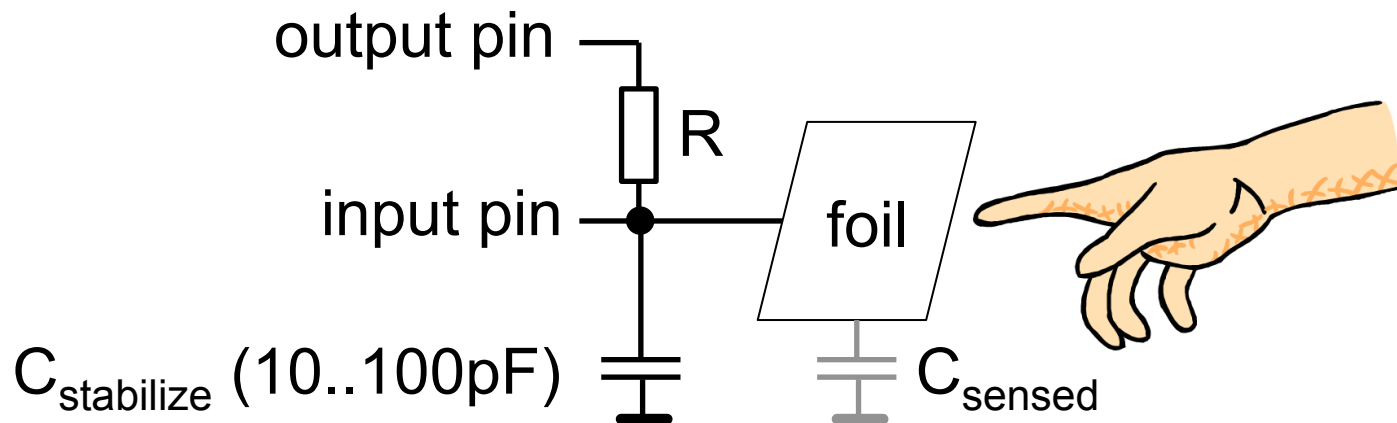- Algorithm
 - Change state of output pin
 - Measure delay in time of input pin (loop)
- Principle
 - Capacitor is charged / discharged over time
 - Time depends on R and C_{sensed}



Light-to-Voltage Sensors (TSL250R)

- Converts light intensity to voltage
- Photodiode + OpAmp
- Supply-voltage range: 2.7..5.5V
- Supply current: 1.1 mA


 
 
 
 



Figure sources: TAOS Datasheet

Infrared Distance Sensors

 - An emitter sends out light pulses
- A linear CCD array receives reflected light
- Distance corresponds to position on CCD array



Infrared Distance Sensors

 

- Sharp GP2Y0A21YK0F
 - Distance: 10 to 80 cm
 - Near infrared: $\lambda = 870$ nm
 - Operation: 5V, 30mA
 - Connectors: Vcc, GND, Vout
- Needs significant current
 - Put large capacitor between Vcc and GND
- Linearizing analog output
 - distance = $27.93 * V_{out}^{-1.2}$
 - piecewise linear interpolation

 


Figure sources: Sharp Datasheet

Force Sensing Resistors (FSRs)

- Force Sensing Resistors
 - Composed of multiple layers
 - Flat, sensitive to bend
 - Force changes resistance
 - Non-linear response curve

- Example: Interlink FSR-402

 
 
 


Figure 1: FSR Construction

FSR Characteristics

- Low force range 0..1kg important for human interaction
- Not very precise: force accuracy 5..25%
- But humans are even worse in judging pressure


 
 
 


Figure sources: Interlink

FSR Interface Circuits

 - Voltage divider
 - Very nonlinear
 - Behaves like switch



- Current-to-voltage converter
 - Better dynamic range

 
 


Figure sources: Interlink

FSR Shapes

- Examples from Interlink


 


Figure sources: Interlink

FSR Bend Sensors

 - Change resistance when bent
- Un-flexed: 10k Ω Flexed / bent 90°: 30..40k Ω



- Sensor glove
 - <http://www.tufts.edu/programs/mma/emid/projectreportsS04/moerlein.html>



<http://www.tufts.edu/programs/mma/emid/projectreportsS04/moerlein.html>

Temperature Sensor (Analog Devices AD22100)

- Temperature range:
−50°C to +150°C
- Accuracy: < ±2%
- Linearity: < ±1%
- Output:

$$V_{OUT} = 1.375 \text{ V} + T * 0.0225 \text{ V/}^\circ\text{C}$$

 
 
 


Figure sources: AnalogDevices Datasheet

Air Pressure Sensors (MPX 4115A)

- Senses absolute air pressure in altimeter or barometer applications
- High level analog output signal
- Temperature compensation


 
 


Figure sources: Motorola Datasheet

Piezo Elements as Sensors



- Piezo elements can be used for output, but also for sensing vibration, e.g. knocks
 - Generates voltage when deformed by vibration, sound wave, mechanical strain
 - Generates vibration (a sound), when voltage is applied
- Directly usable as sensor by reading analog value with AVR's ADC
- Piezos are polarized (red = V_{CC} , blue = ground)
- Need a current-limiting resistor ($1M\Omega$)
- Glue against sensing surface

 

© Stefan Riepl (Quark48), CC-BY-SA

Accelerometer ADXL335

 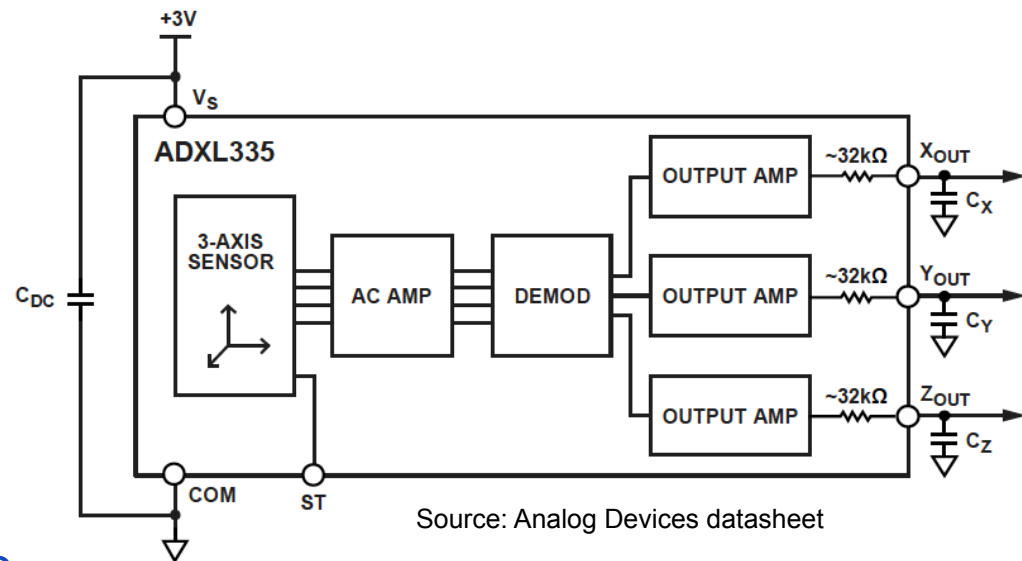
- Polysilicon surface-micromachined sensor
- 3-axis sensing, $\pm 3g$
 - Gravity as static reference
- Low power ($350\mu A @ V_{CC} = 3V$)
- Output voltages X_{out} , Y_{out} , Z_{out} proportional to acceleration
- Selectable bandwidth / filtering
 - Capacitors C_X , C_Y , C_Z
 - $F_{-3dB} = 1 / (2\pi (32k\Omega) C_{(X, Y, Z)})$
 - Max: 1600 Hz (x,y axes), 500 Hz (z axis)




Source: Analog Devices datasheet

How do Accelerometers work?

- Causes of acceleration
 - Gravity, vibration, human movement, etc.
- Operating principle
 - Conceptually: damped mass on a spring
 - Typically: silicon springs anchor a silicon wafer to controller
 - Movement to signal: Capacitance, induction, piezoelectric etc.
- For ADXL335
 - Polysilicon surface-micromachined structure containing mass
 - Polysilicon springs suspend mass
 - Deflection of mass measured with differential capacitor: one plate fixed, other attached to moving mass
 - Square waves drive plates
 - Deflection unbalances differential capacitor

 


Gyroscope IDG500

 

Source: InvenSense datasheet

- Dual-axis angular rate sensor (gyroscope)
 - Senses rate of rotation about X- and Y-axis (in-plane sensing)
 - Factory-calibrated
 - Low-pass filters

- $V_{CC} = 3V$

 

Source: InvenSense datasheet

- Output voltage proportional to the angular rate
- Separate outputs for standard and high sensitivity
 - X-/Y-Out Pins: 500°/s full scale range, 2.0mV/°/s sensitivity
 - X/Y4.5-Out Pins: 110°/s full scale range, 9.1mV/°/s sensitivity


I2C Magnetometer / Compass Honeywell HMC6352

- Compass module
 - 2-axis magneto-resistive sensors
 - Support circuits
 - Algorithms for heading computation

- Parameters

- $V_{CC} = 2.7..5.2V$, typ. 3.0V
- Update rate: 1..20Hz
- Heading resolution: 0.5°
- I2C interface

 used for complex sensors
(e.g., allows sending
configuration commands)



Source: Honeywell datasheet

 



Figure 1
Reference Design Schematic

Source: Honeywell datasheet

ANALOG TO DIGITAL CONVERSION

AVR ATtiny45 Architecture

- Analog to Digital Converter

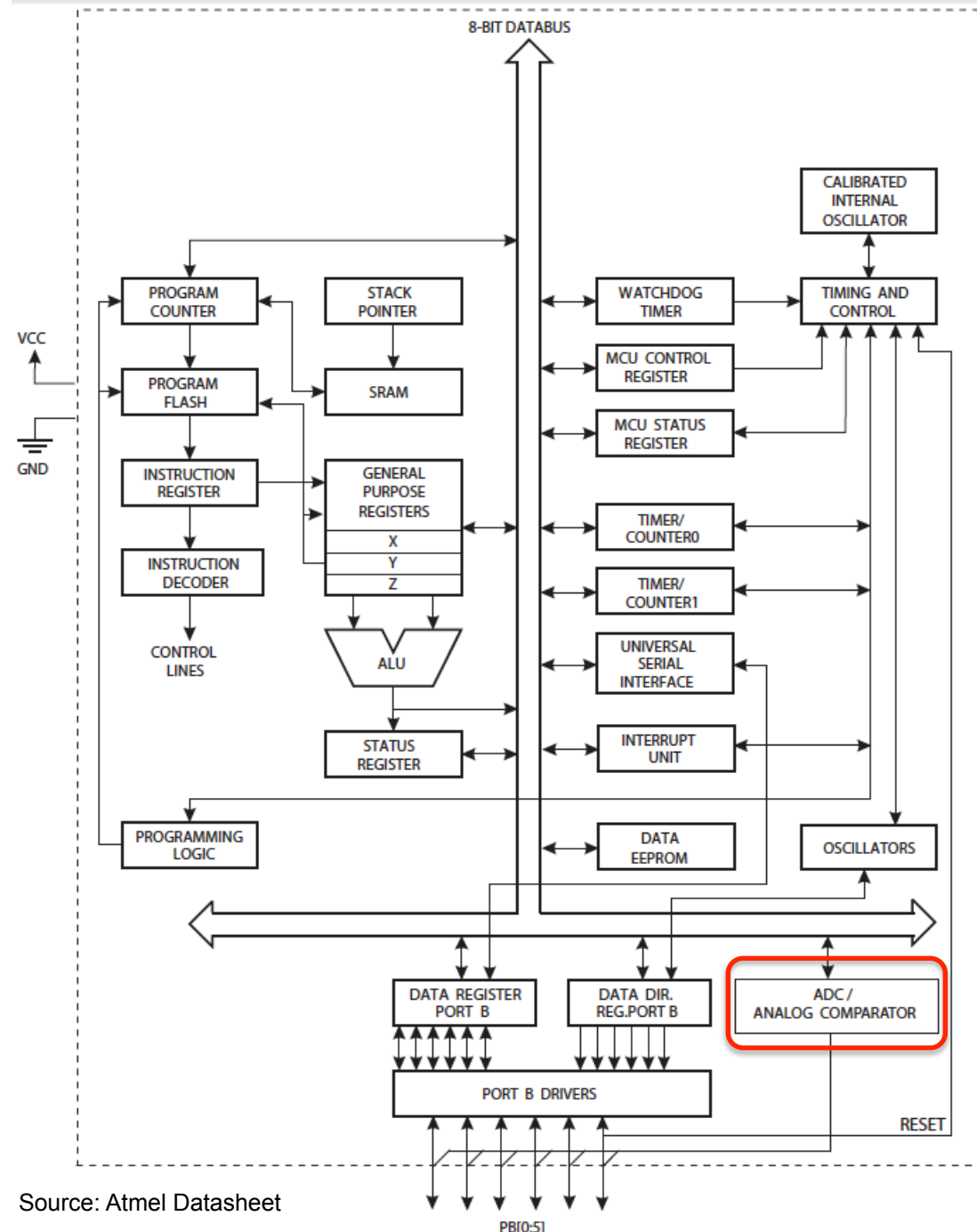


Source: Atmel Datasheet

PB10-51

Analog to Digital Converter

- Converts analog input voltage to 10-bit digital value
 - $\text{value} = 1024 * V_{\text{IN}} / V_{\text{REF}}$
 - Min analog value = ground
 - Max analog value = V_{CC}
 - Reference voltage: 1.1V or 2.56V or external reference or V_{CC}
 - 0x000 = ground
 - 0x3ff = ref. voltage - one LSB
- Characteristics
 - 4 input channels
 - 65-260 μs conversion time
 - 15kSPS conversion rate
(SPS = samples per second)

 

Analog to Digital Converter Registers

- ADMUX – ADC Multiplexer Selection Register

| | | | | | | | | | | | | | | | | | |
|---------------|---|-------|-------|------|------|------|------|-----|-------|-------|-------|-------|------|------|------|------|-------|
| Bit | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | | | | | | | | | |
| 0x07 | <table border="1"><tr><td>REFS1</td><td>REFS0</td><td>ADLAR</td><td>REFS2</td><td>MUX3</td><td>MUX2</td><td>MUX1</td><td>MUX0</td></tr></table> | | | | | | | | REFS1 | REFS0 | ADLAR | REFS2 | MUX3 | MUX2 | MUX1 | MUX0 | ADMUX |
| REFS1 | REFS0 | ADLAR | REFS2 | MUX3 | MUX2 | MUX1 | MUX0 | | | | | | | | | | |
| Read/Write | R/W | R/W | R/W | R/W | R/W | R/W | R/W | R/W | | | | | | | | | |
| Initial Value | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | | | | | | | | | |

Source: Atmel Datasheet

- MUX0..1: Selecting input channel (00=ADC0, ... , 11=ADC3)
- REFS0..1: Internal reference (0: V_{CC} , 1: external ref. at PB0, 2: internal ref. 1.1V)
- ADLAR: ADC left adjust result (1 = left adjust result)

Analog to Digital Converter Registers

- ADCL and ADCH – The ADC Data Register, ADLAR = 0

| | | | | | | | | |
|------|------|------|------|------|------|------|------|------|
| 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | |
| – | – | – | – | – | – | ADC9 | ADC8 | ADCH |
| ADC7 | ADC6 | ADC5 | ADC4 | ADC3 | ADC2 | ADC1 | ADC0 | ADCL |
| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | |

Source: Atmel Datasheet

- ADCL and ADCH – The ADC Data Register, ADLAR = 1


| | | | | | | | | |
|------|------|------|------|------|------|------|------|------|
| 15 | 14 | 13 | 12 | 11 | 10 | 9 | 8 | |
| ADC9 | ADC8 | ADC7 | ADC6 | ADC5 | ADC4 | ADC3 | ADC2 | ADCH |
| ADC1 | ADC0 | – | – | – | – | – | – | ADCL |
| 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | |

Source: Atmel Datasheet

- If left adjusted: read ADCH to get 8-bit precision

Analog to Digital Converter Registers

 - ADCSRA – ADC Control and Status Register A




Source: Atmel Datasheet

- ADEN: ADC enable (1 = on, 0 = off)
- ADSC: ADC start conversion, write 1 to start conversion
 - Reads as 1 while conversion in progress
- ADATE: ADC auto trigger enable, write 1 to enable triggering on positive edge of trigger signal
- ADIF: ADC interrupt flag, set when conversion complete
- (continued on next slide...)

Analog to Digital Converter Registers

 - ADCSRA – ADC Control and Status Register A



Source: Atmel Datasheet

- ...
- ADIE: ADC interrupt enable, write 1 (and set I-bit in SREG) to enable “ADC complete interrupt”
- ADPS2:0: ADC prescaler select bits, division factor of system clock to ADC clock
0..7: 2, 2, 4, 8, 16, 32, 64, 128

Analog to Digital Converter Registers

- ADCSR_B – ADC Control and Status Register B

| Bit | 7 | 6 | 5 | 4 | 3 | 2 | 1 | 0 | |
|---------------|------------|-------------|------------|---|---|--------------|--------------|--------------|--------------------|
| 0x03 | BIN | ACME | IPR | – | – | ADTS2 | ADTS1 | ADTS0 | ADCSR _B |
| Read/Write | R/W | R/W | R/W | R | R | R/W | R/W | R/W | |
| Initial Value | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | |


Source: Atmel Datasheet

- ADTS_{2..0}: ADC auto trigger source, triggers conversion on rising edge of selected interrupt

| ADTS ₂ | ADTS ₁ | ADTS ₀ | Trigger Source |
|-------------------|-------------------|-------------------|-------------------------------|
| 0 | 0 | 0 | Free Running mode |
| 0 | 0 | 1 | Analog Comparator |
| 0 | 1 | 0 | External Interrupt Request 0 |
| 0 | 1 | 1 | Timer/Counter Compare Match A |
| 1 | 0 | 0 | Timer/Counter Overflow |
| 1 | 0 | 1 | Timer/Counter Compare Match B |
| 1 | 1 | 0 | Pin Change Interrupt Request |

Analog to Digital Converter Registers

 - DIDR0 – Digital Input Disable Register 0



Source: Atmel Datasheet

- Write 1 to disable unneeded ADC input channels
- Reduces power consumption

Starting an Analog-to-Digital Conversion

- Starting a single conversion
 - Write 1 to start conversion bit (ADSC) in control register (ADCSRA)
 - ADSC reads 1 during conversion
- Auto triggering
 - Various sources (e.g. timer for fixed intervals)
 - Interrupt flag for source will be set and conversion triggered, even if interrupt is disabled, flag must be cleared to trigger subsequent conversion
 - Free-running-mode: start new conversion as soon as ongoing conversion has finished

Conversion Timing

- Input clock frequency
 - 50..200 kHz ADC for maximum resolution
 - >200kHz if lower resolution sufficient
- Duration
 - Normal conversion takes 13 ADC clock cycles
 - Initial conversion 25 ADC clock cycles
- Discard first result after ADC activation or chg. ref.
 - Result may be wrong → discard

Analog Input Signal


- Signal should be slowly varying
- Signal components higher than the Nyquist frequency ($f_{\text{ADC}} / 2$) should not be present
- Recommendations
 - Keep signal paths short
 - Separate analog tracks from digital tracks
 - Do not switch digital output pin during conversion
 - Place bypass capacitors close to V_{CC} and GND pins
 - Use ADC Noise Reduction Mode for higher accuracy

Example: 10kΩ Poti on ADC1 (PB2)

```
#include <avr/io.h>
#include <util/delay.h>
static unsigned char ledState = 0;


void blinkLed(unsigned int d) {
    ledState = 1 - ledState;
    if (ledState) PORTB |= 0x01;
    else PORTB &= 0xfe;
    _delay_ms(d);
}

int main() {
    // next slide...
}
```

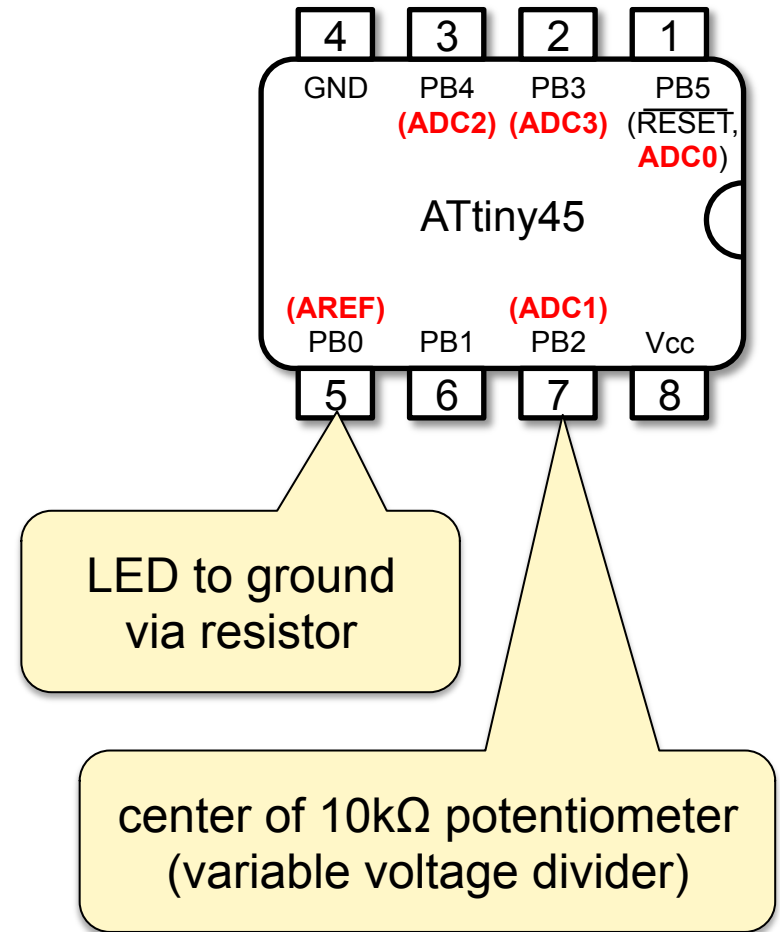

 Example: 10kΩ Poti on ADC1 (PB2)

```
int main() {  
    DDRB  &= 0b11111011; // port 2 as input  
    PORTB &= 0b11111011; // port 2 disable pull-up
```




```
    ADMUX = (0 << REFS0) | (1 << ADLAR) | 1; // Vcc, left adj., ADC1 = PB2  
    ADCSRA = (1 << ADEN) | 6; // enable, prescaler 1:64 (150kHz)  
    ADCSRB = 0; // free running mode  
    DIDR0 = (1 << ADC0D) | (1 << ADC2D) | (1 << ADC3D);  
           // disable ADCs 0, 2, 3
```

```
while (1) {  
    ADCSRA |= (1 << ADSC); // start conversion  
    while (ADCSRA & (1 << ADSC)); // wait until conversion complete  
    unsigned int d = ADCH;  
    blinkLed(d); // use value...  
}
```


UNIVERSAL SERIAL BUS (USB)

Universal Serial Bus (USB)

 - High data rates (difficult to process with ATtinys)
 - USB 1.0: 1.5 Mbit/s (Low-Speed) and 12 Mbit/s (Full-Speed)
 - USB 2.0: 480 Mbit/s (High-Speed)
 - USB 3.0: 5 Gbit/s (Super-Speed)




- 500mA max. (at $V_{CC} = 5V$)
- Some AVR's have built-in USB modules
 - the ones we use don't

| | |
|-------|-----------------|
| Pin 1 | V_{CC} (+5 V) |
| Pin 2 | Data- |
| Pin 3 | Data+ |
| Pin 4 | Ground |

USB-to-Serial Converter

 - Serial side (RS232)
 - RTS (request-to-send, green)
 - RX (receive, yellow)
 - TX (transmit, orange)
 - 5V (red)
 - CTS (clear-to-send, brown)
 - GND (black)



- Virtual COM Port Drivers
 - www.ftdichip.com/Drivers/VCP.htm

FTDI FT232RQ Virtual COM Port Drivers

- Virtual COM port drivers
 - <http://www.ftdichip.com/Drivers/VCP.htm>
- USB device appears as virtual COM port


`cd /dev`

`ls -l | grep usb`

`cu.usbserial-A100XPZ`

`tty.usbserial-A100XPZ`

- Shows up in System Profiler

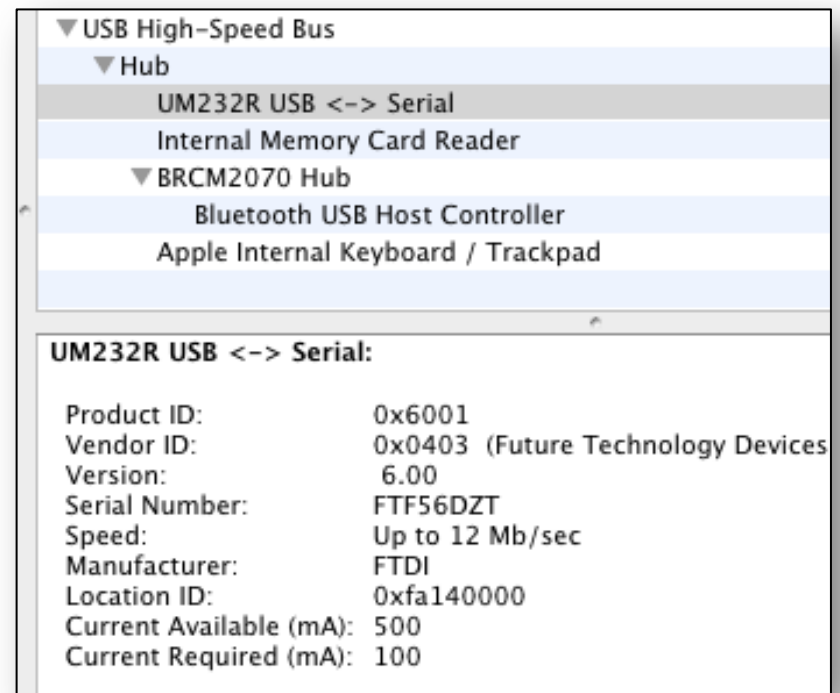


Using Virtual COM Port in Java

- Requires Java Serial Communications API
 - http://download.oracle.com/docs/cd/E17802_01/products/products/javacomm/reference/api/index.html
 - various implementations
- Windows
 - <http://www.oracle.com/technetwork/java/index-jsp-141752.html>
 - [javacomm20-win32.zip](#)
- Mac OS X, Linux
 - <http://rxtx.qbang.org/wiki/index.php/Download>
 - http://rxtx.qbang.org/wiki/index.php/Using_RXTX
- Add jar to Eclipse project
 - Properties, Java Build Path, Add External JARs...
 - RXTXcomm.jar (or other implementation)

Using Virtual COM Port in Java, Eclipse

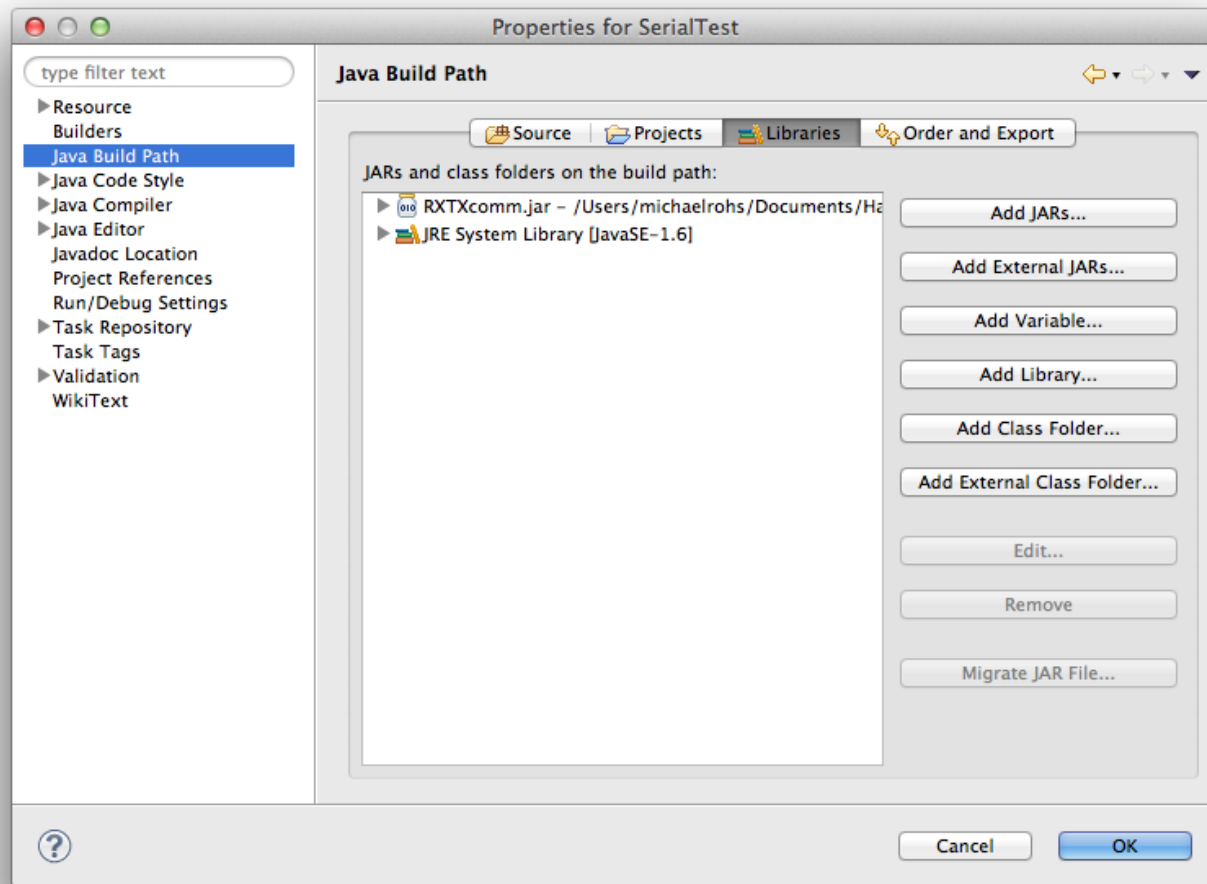- Properties, Java Build Path, Add External JARs...



Example: Sending to Virtual Com Port in Java

```
import java.io.*;      import java.util.*;      import gnu.io.*;

public class Usb2Serial {
public static void main(String[] args) throws Exception {
    Enumeration ports = CommPortIdentifier.getPortIdentifiers();
    while (ports.hasMoreElements()) {
        CommPortIdentifier portId = (CommPortIdentifier) ports.nextElement();
        if (portId.getPortType() == CommPortIdentifier.PORT_SERIAL) {
            if (portId.getName().equals("/dev/tty.usbserial-A100OXPZ")) {
                SerialPort sp = (SerialPort) portId.open("Usb2Serial", 2000);
                OutputStream os = sp.getOutputStream();
                sp.setSerialPortParams(9600,
                    SerialPort.DATABITS_8,
                    SerialPort.STOPBITS_1,
                    SerialPort.PARITY_NONE);

                os.write("hello world".getBytes());
                try { Thread.sleep(2000); } catch (InterruptedException ex) {}
                sp.close();
            }
        }
    }
}
```

replace by actual device name

ATmega8 Echo Server

- PINs

- PD0 (RXD) to TX (transmit, orange)
- PD1 (TXD) to RX (receive, yellow)

- Source

```
#include "usart.h"
```

```
int main() {
```

```
    // baud rate = clock / (16 * (brr+1))
```

```
    USART_Init(51); // 51: 9600 baud @ 8MHz clock
```

```
    while (1) {
```

```
        unsigned char x = USART_Receive();
```


```
        USART_Transmit(x);
```

```
    }
```

```
    return 0;
```

```
}
```

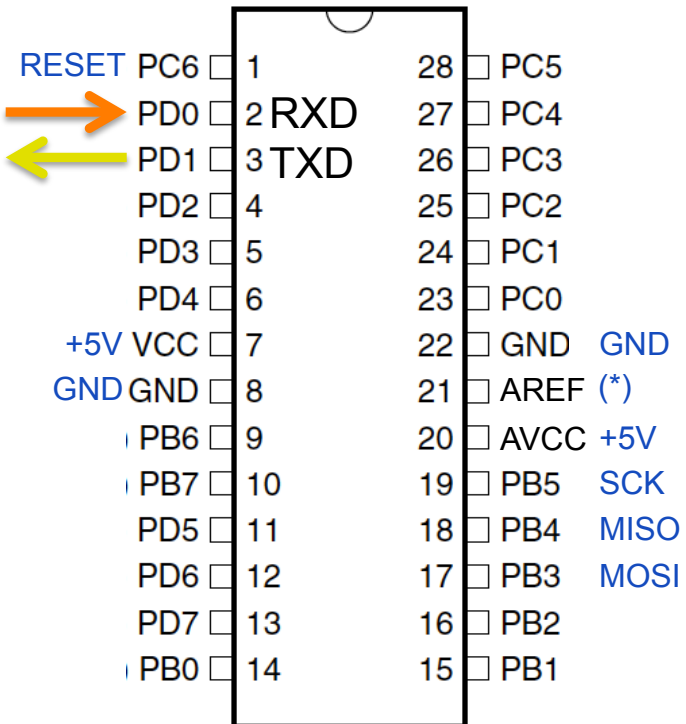TX (transmit, orange) →
RX (receive, yellow) ←



Source: Atmel Datasheet

(*) a small capacitor (100nF) between AREF and GND improves noise immunity of the A/D converter

ATmega8 Fuses for EchoServer

- low: 0xE4
- high: 0xDF

Device selection

Select the AVR device type you want to configure. When changing this setting, default fuse settings will automatically be updated. The default fuse settings (hexadecimal representation of the fuse settings) can be reviewed and even be set in the last form at the bottom of the page.


AVR part name: (141 parts currently listed)

Feature configuration

This allows easy configuration of your AVR device. All changes will be applied instantly.

Features

| |
|---|
| <input type="text" value="Int. RC Osc. 8 MHz; Start-up time: 6 CK + 64 ms; [CKSEL=0100 SUT=10]"/> |
| <input type="checkbox"/> Brown-out detection enabled; [BODEN=0] |
| <input type="text" value="Brown-out detection level at VCC=2.7 V; [BODLEVEL=1]"/> |
| <input type="checkbox"/> Boot Reset vector Enabled (default address=\$0000); [BOOTRST=0] |
| <input type="text" value="Boot Flash section size=128 words Boot start address=\$0F80; [BOOTSZ=11]"/> |
| <input type="checkbox"/> Preserve EEPROM memory through the Chip Erase cycle; [EESAVE=0] |
| <input type="checkbox"/> CKOPT fuse (operation dependent of CKSEL fuses); [CKOPT=0] |
| <input checked="" type="checkbox"/> Serial program downloading (SPI) enabled; [SPIEN=0] |
| <input type="checkbox"/> Watch-dog Timer always on; [WDTON=0] |
| <input type="checkbox"/> Reset Disabled (Enable PC6 as i/o pin); [RSTDISBL=0] |

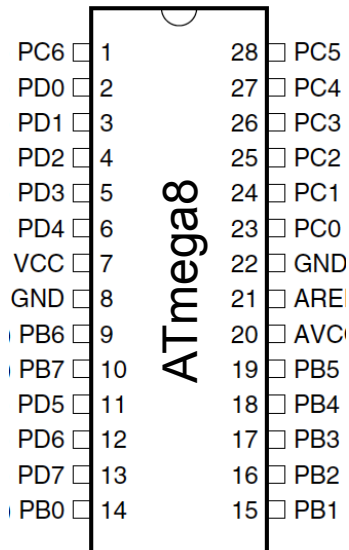

Source: Atmel Datasheet

Source: www.engbedded.com/fusecalc/

ATmega8 USART Initialization

```
void USART_Init(unsigned int brr)
{
    // set baud rate: baud = clock / (16 * (brr+1)) <=> brr = clock / (16 * baud) - 1
    UBRRH = (brr >> 8) & 0x0f;
    UBRRL = brr;

    // enable receiver and transmitter
    UCSRB = (1 << RXEN) | (1 << TXEN) | (0 << UCSZ2);

    // set frame format: 8 data bits, no parity, 1 stop bit
    UCSRC = (1 << URSEL) | (0 << UMSEL) | (0 << UPM0) |
           (0 << USBS) | (3 << UCSZ0) | (0 << UCPOL);
}
```

ATmega8 USART Transmission

```
void USART_Transmit(unsigned char data) {  
    // wait until data register empty  
    while (!(UCSRA & (1<<UDRE)));  
    // send the data  
    UDR = data;  
}
```


```
unsigned char USART_Receive() {  
    // wait for data to be received  
    while (!(UCSRA & (1<<RXC)));  
    // return the data  
    return UDR;  
}
```

ATmega8 USART Transmission


```
void USART_Transmit_String(unsigned char* data)
{
    unsigned char c;
    while ((c = *data++) != 0) {
        USART_Transmit(c);
    }
}
```

Universal Asynchronous Receiver/Transmitter (UART)

 - Sequential transmission/reception of a sequence of bits
- Framing (start bit = 0, stop bit = 1; 8 data bits, no parity bit)



- Timing diagram

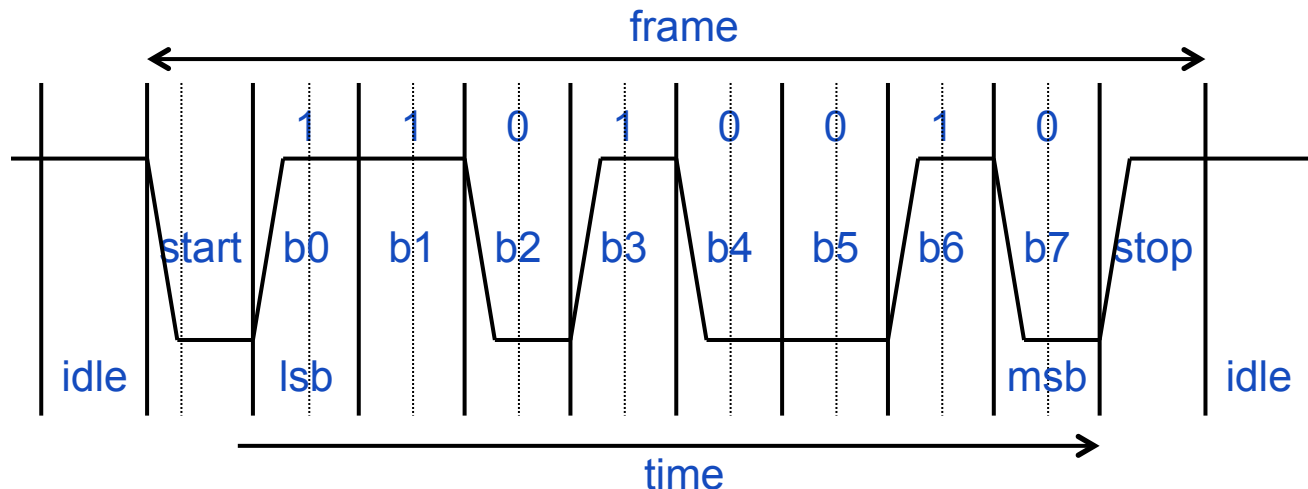


- Hardware handshake: Request-to-send, clear-to-send

ATmega8 USART

- USART = Universal Synchronous and Asynchronous serial Receiver and Transmitter
 - asynchronous: no clock signal, common baud rates, each frame synchronized
 - synchronous: clock signal
 - full duplex: simultaneous transmission and reception
 - frames formats: 5..9 data bits, 1..2 stop bits
 - parity generation / check (even: xor of data bits, odd: *not* even)
 - data overrun and framing error detection
 - interrupts: TX complete, TX data register empty, RX Complete
 - multi-processor communication


ATmega8 USART Block Diagram

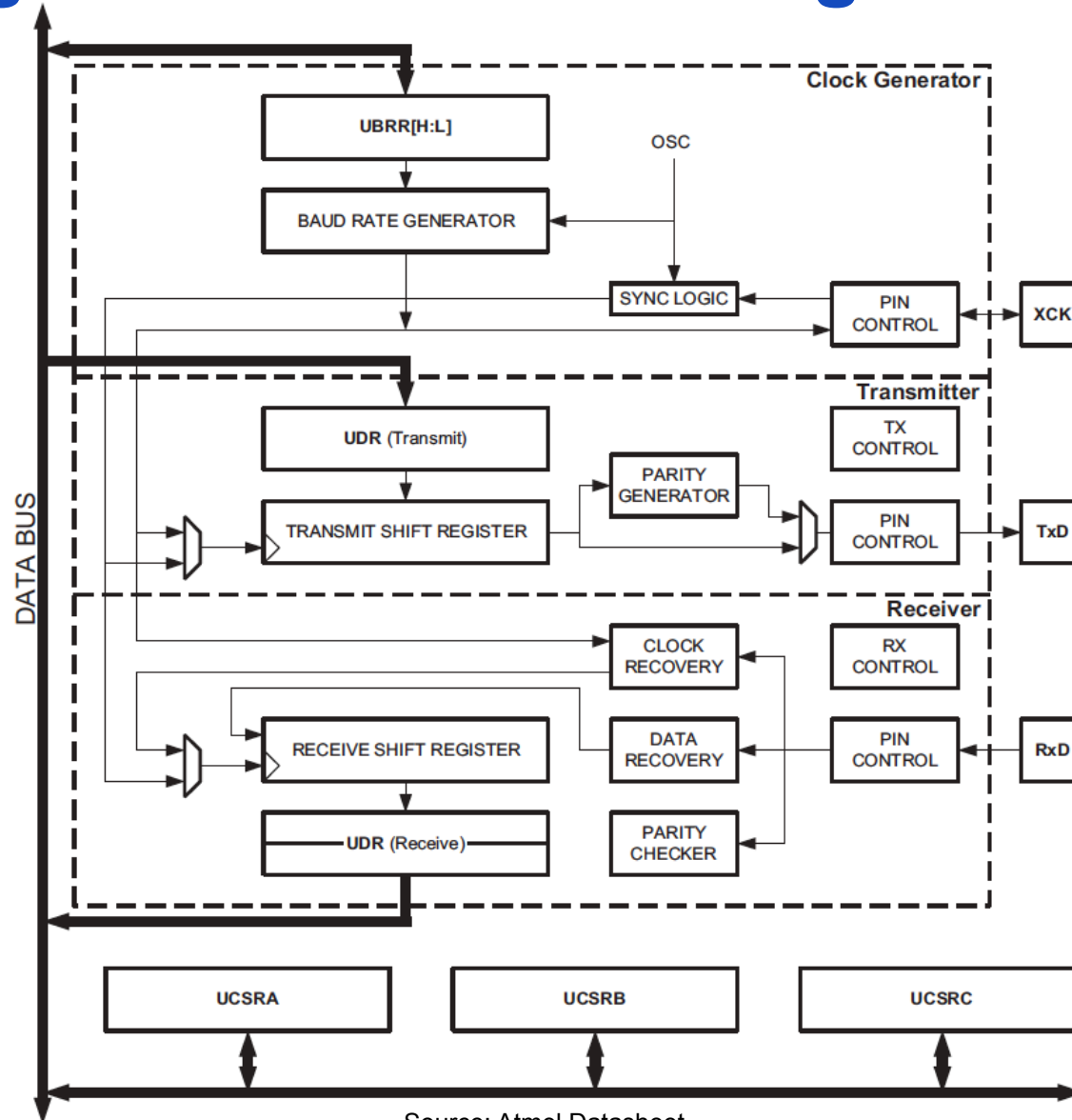


Source: Atmel Datasheet

ATtiny2313 USART Bit Sampling

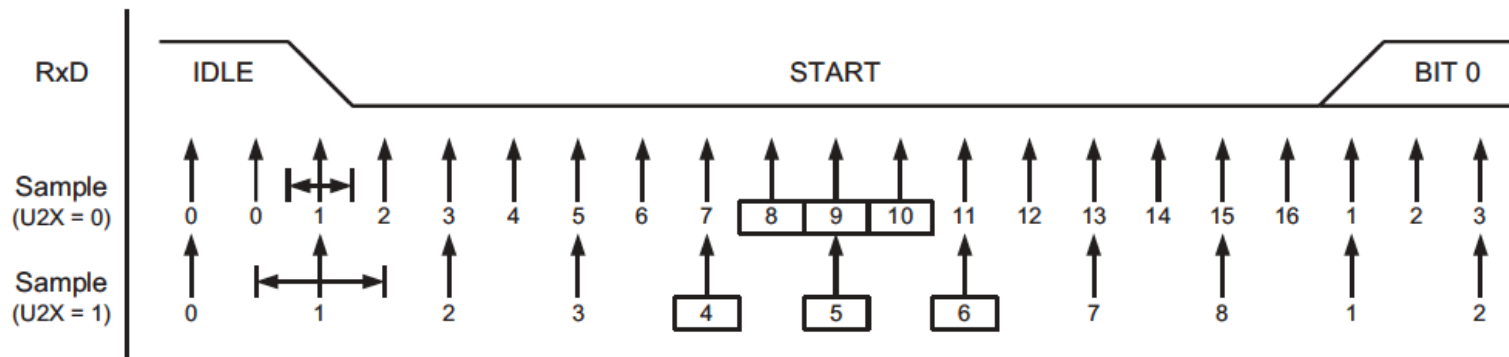- Single (U2X = 0) and double speed (U2X = 1) modes
- Double speed: majority vote on three samples
- Start bit:



- Data bits:

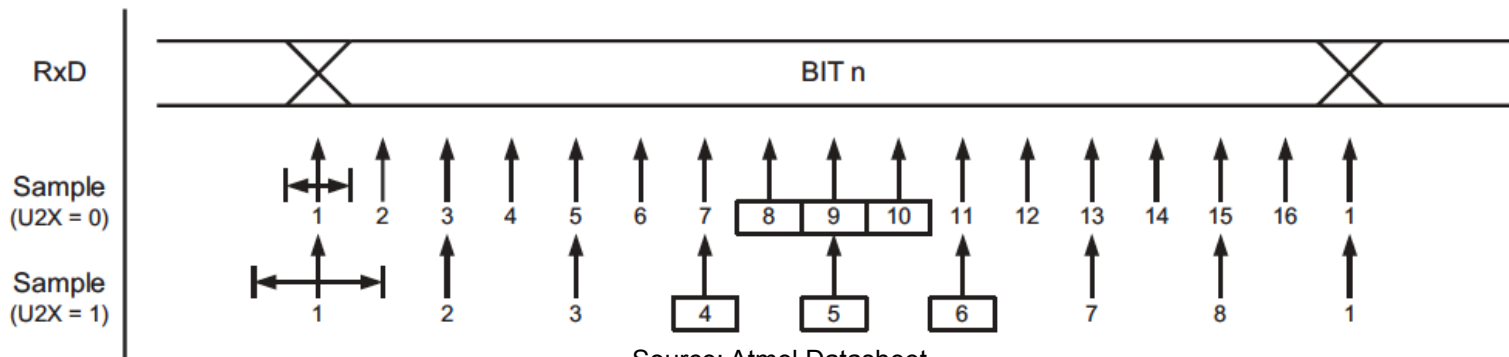

Source: Atmel Datasheet

ATmega8 USART Baud Rates

- UBRR = baud rate register (12 bits)
- Baud rate computation
 - asynchronous, normal: $baud = \frac{f_{osc}}{16 (UBRR + 1)} \Leftrightarrow UBRR = \frac{f_{osc}}{16 \text{ baud}} - 1$
 - asynchronous, double: $baud = \frac{f_{osc}}{8 (UBRR + 1)} \Leftrightarrow UBRR = \frac{f_{osc}}{8 \text{ baud}} - 1$
 - synchronous master: $baud = \frac{f_{osc}}{2 (UBRR + 1)} \Leftrightarrow UBRR = \frac{f_{osc}}{2 \text{ baud}} - 1$
- Maximum baud rate error should be $\pm 2.0\%$ (8 data bits)
- Example: $f_{osc} = 16\text{MHz}$, $baud = 115200$:

$$UBRR = \frac{16 \cdot 10^6}{16 \cdot 115200} - 1 \approx 7.68, \quad baud = \frac{16 \cdot 10^6}{16 \cdot (8 + 1)} \approx 111111.11 \quad \rightarrow -3.5\% \text{ error}$$

BRAINSTORMING

Brainwriting (in your group)

- Repeat 5 rounds
 - 3 minutes: On paper, fill one row with 3 ideas
 - Pass on paper clockwise
 - Read other ideas, fill next line with 3 more ideas
- Select the 3 best ideas
 - 10 minutes
 - Present selected ideas

| | | |
|--|--|--|
| | | |
| | | |
| | | |
| | | |
| | | |